Eingangsimpedanz

$$\underline{Z}_{\rm i} \,=\, \frac{\underline{v}_1}{\underline{i}_1} \,=\, \frac{1+\underline{y}_{22}\underline{Z}_{\rm L}}{\underline{y}_{11}+\Delta_y\underline{Z}_{\rm L}} \,=\, \frac{\underline{h}_{11}+\Delta_h\underline{Z}_{\rm L}}{1+\underline{h}_{22}\underline{Z}_{\rm L}} \;,$$
 die Ausgangsimpedanz ($\underline{v}_0=0$)

 $\underline{Z}_{\rm o} = \frac{\underline{v}_2}{\underline{i}_2} \; = \; \frac{1 + \underline{y}_{11} \underline{Z}_{\rm G}}{y_{22} + \Delta_y \underline{Z}_{\rm G}} \; = \; \frac{\underline{h}_{11} + \underline{Z}_{\rm G}}{\Delta_h + \underline{h}_{22} \underline{Z}_{\rm G}} \; , \label{eq:Z_o}$

 $\underline{H}_i = \frac{\underline{i}_2}{\underline{i}_1} = \frac{\underline{y}_{21}}{y_{11} + \Delta_y Z_L} = \frac{\underline{h}_{21}}{1 + \underline{h}_{22} Z_L}$

 $\underline{H}_v \; = \; \frac{\underline{v}_2}{\underline{v}_1} \; = \; \frac{-\underline{y}_{21}\underline{Z}_{\mathrm{L}}}{1 + \underline{y}_{22}\underline{Z}_{\mathrm{L}}} \; = \; \frac{-\underline{h}_{21}\underline{Z}_{\mathrm{L}}}{\underline{h}_{11} + \Delta_h\underline{Z}_{\mathrm{L}}} \; .$